

ARJUN MENON V

EE18B104

EE632D - RF Integrated Circuits

ANALYSIS

Assignment 1

1. (a)  $P_{out} = 1W$  (desired),  $R_{ant} = 50\Omega$  ( $= R_s$ )  
 $f_{op} = 1GHz$

W/o Matching Network

$$P_{max} = \frac{V_{rms}^2}{R_s} = \left(\frac{5}{2}\right)^2 \times \frac{1}{2 \times 50} W = \frac{6.25}{100} W$$


$$P_{max} = 62.5mW$$

(b) Desired impedance =  $R_{des}$

$$P = 1W = \frac{V_{rms}^2}{R_{des}} = \frac{1}{2} \times \frac{2.5^2}{R_{des}}$$

$$R_{des} = \frac{2.5^2}{2} = 3.125\Omega$$

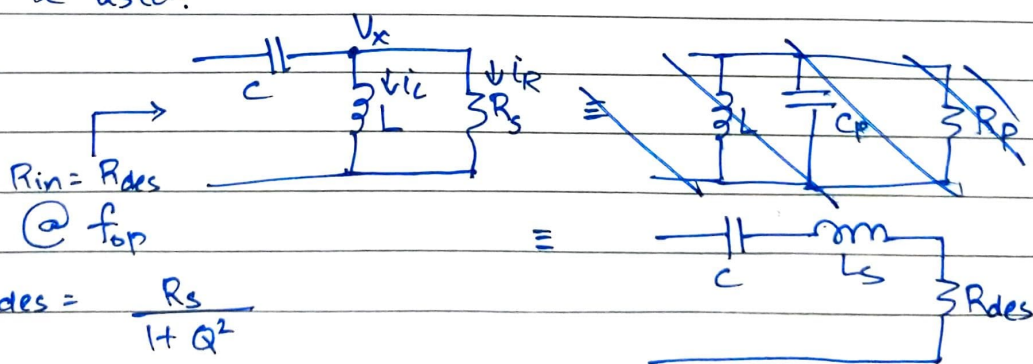(c)  $\because R_{des} < R_s$ , the following L-match network must be used:



$$R_{des} = \frac{R_s}{1+Q^2}$$

$$Q = \frac{\omega_0 \times \frac{1}{2} L i_L^2}{\frac{1}{2} R_s i_R^2}$$

$$\omega_0 = \frac{1}{\sqrt{C L_s}}$$

$$= \frac{\omega_0 L}{R_s} \left( \frac{V_x}{\omega_0 L} \right)^2 \left( \frac{R_s}{V_x} \right)^2 = \frac{R_s}{\omega_0 L} = Q_{series} = \frac{\omega_0 L_s}{R_{des}} = \frac{1}{\omega_0 C R_{des}}$$

$$\frac{\omega_0 L_s}{R_{des}} = \frac{R_s}{\omega_0 L} \Rightarrow L_s = \frac{R_s R_{des}}{\omega_0^2 L} = \frac{R_s^2}{\omega_0^2 L (1+Q^2)} = \frac{L Q^2}{1+Q^2}$$

Further,

$$\frac{R_s}{\omega_0 L} = Q = \frac{1}{\omega_0 C R_{des}}$$

$$C = \frac{\omega_0 L}{\omega_0 R_{des} R_s}$$

$$= \frac{L}{R_s R_{des}}$$

$$\omega_0 = \frac{1}{\sqrt{L_s C}}$$

→ so that  $Z_{in} @ \omega_0 = R_{des}$

$$R_{des} = 3.125 \Omega$$

$$R_s = 50 \Omega$$

$$1 + Q^2 = \frac{R_s}{R_{des}} = \frac{50}{3.125} = 16$$

$$Q = \sqrt{15} = 3.87298$$

$$L_s C = L \left( \frac{Q^2}{1 + Q^2} \right) = \frac{L}{50 \times 3.125}$$

$$= L^2 \left( \frac{15}{16} \right) \times \frac{1}{156.25} = L^2 \times 6 \times 10^{-3}$$

$$L_s C = \frac{1}{\omega_0^2} = \frac{1}{4\pi^2 f_0^2} = \frac{1}{4 \times \pi^2 \times 10^{18}}$$


$$L^2 \times 6 \times 10^{-3} = \frac{1}{3.94784 \times 10^{19}}$$

$$L^2 = 4.2217 \times 10^{-18} \text{ H}^2$$

$$L = 2.0547 \text{ nH}$$

$$C = \frac{2.0547 \times 10^{-9}}{50 \times 3.125} \text{ F} = 13.15 \text{ pF}$$

L-match: 13.15 pF

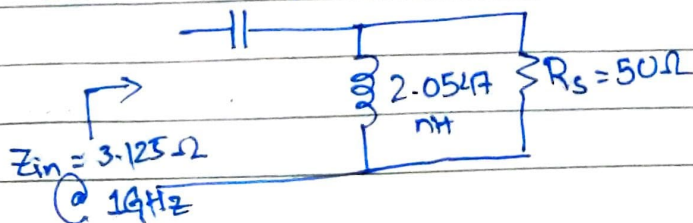

d) Theoretical 3-dB BW:

$$Q = \frac{\omega_0}{3\text{dB BW}}$$

$$3\text{dB BW} = \frac{\omega_0}{\sqrt{15}} = \frac{2\pi \times 10^9}{3.87298} \text{ Hz}$$

$$BW = 622 \text{ GHz}$$

$$BW \text{ in Hz} = \frac{f_0}{Q} \text{ Hz}$$

$$BW = 2.58199 \times 10^8 \text{ Hz}$$


$$BW = 258.199 \text{ MHz} \rightarrow \text{theoretical}$$

$$BW \text{ from simulation: } 255.956 \text{ MHz}$$

$$Q \text{ from simulation: } 3.9069$$

$$Q \text{ theoretical: } 3.873$$

e) High-pass T-match

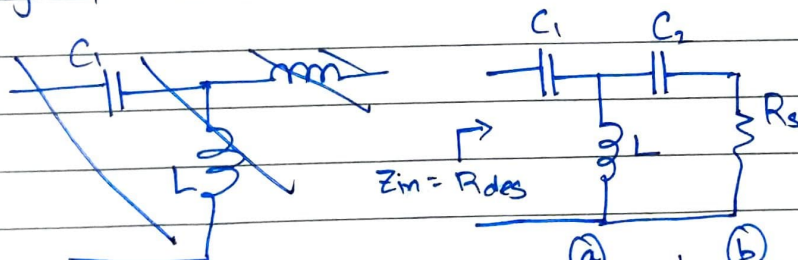

$$Q_L = \frac{R_1}{\omega L_1}; Q_R = \frac{R_1}{\omega L_2}$$

$$Q_{\text{net}} = \frac{\omega \times \frac{1}{2} (L_1 I_1^2 + L_2 I_2^2)}{\frac{1}{2} (I_1^2 R_1)}$$


$$\text{where } I_1 \omega L_1 = I_2 \omega L_2 = V_1 = I_1 R_1$$

$$Q_{\text{net}} = \frac{\omega \left( \frac{I_1^2 R_1^2}{\omega^2} \right) \left( \frac{1}{L_1} + \frac{1}{L_2} \right)}{I_1^2 R_1} = \frac{R_1}{\omega L_1} + \frac{R_1}{\omega L_2}$$

$$Q_{\text{net}} = Q_L + Q_R$$

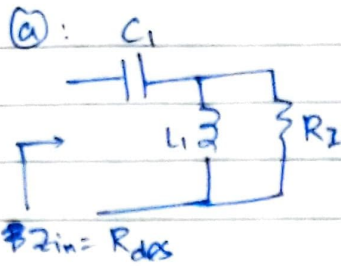
Now, subcircuits (a) and (b) resemble L-matches.





$$R_{des} = \frac{R_I}{1 + Q_L^2}$$

$$Q_L = \sqrt{\frac{R_I}{R_{des}} - 1}$$

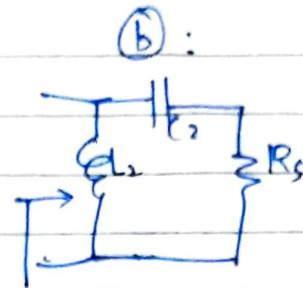


$$R_I = R_S (1 + Q_R^2)$$

$$Q_R = \sqrt{\frac{R_I}{R_S} - 1}$$

$$Q = Q_L + Q_R = 5$$

L-match b:

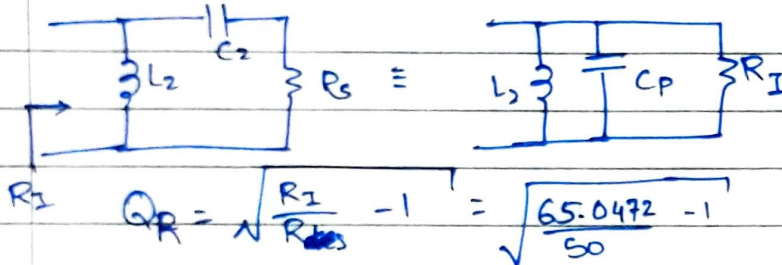

$$Q_R = \sqrt{\frac{R_I}{R_{des}} - 1} = \sqrt{\frac{65.0472}{50} - 1} = 0.5486$$

$$Q_R = \frac{1}{\omega C_2 R_S} = \omega C_P R_I = \frac{R_I}{\omega L_2}$$

$$L_2 = \frac{R_I}{\omega \times Q_R} = \frac{65.0472}{2\pi \times 10^9 \times 0.5486} \text{ H}$$

$$L_2 = 1.88709 \times 10^{-8} \text{ H} = 18.8709 \text{ nH}$$

$$\omega = \frac{1}{\sqrt{L_2 C_P}} \Rightarrow C_P = \frac{1}{\omega^2 L_2} = \frac{10^{-8}}{4\pi^2 \times 10^{18} \times 1.88709}$$

$$= 1.3423 \text{ pF}$$

$$C_2 = \frac{R_I}{\omega^2 L_2^2} = 1.3423 \times 4.32268 \text{ pF}$$

$$C_2 = 5.80233 \text{ pF}$$

$$L_2 = 18.8709 \text{ nH}$$

$$\sqrt{\frac{R_I}{3.125} - 1} + \sqrt{\frac{R_I}{50} - 1} = 5$$

$$\Rightarrow \frac{R_I}{3.125} \left(1 - \frac{1}{R_I}\right) = 25 - 10 \sqrt{\frac{R_I - 1}{50}}$$

$$0.3 R_I = 25 - 10 \sqrt{\frac{R_I - 1}{50}}$$

$$100 \left(\frac{R_I - 1}{50}\right) = 625 - 15 R_I + 0.09 R_I^2$$


$$0.09 R_I^2 - 17 R_I + 725 = 0$$

$$R_I = 123.842 \Omega \text{ or } R_I = 65.0472 \Omega$$

$$\text{Results in } \sqrt{\frac{R_I}{R_{des}} - 1} > 5$$

$$\therefore R_I = 65.0472 \Omega$$

L-match a:

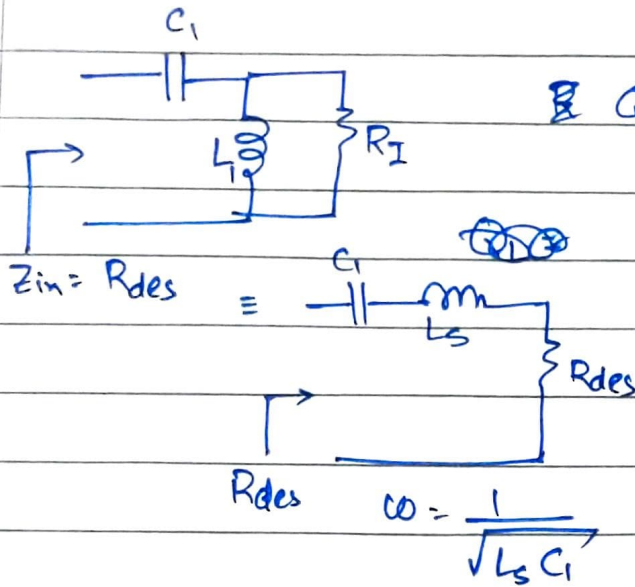

$$Q_L = \sqrt{\frac{R_L}{R_{des}}} = 4.45142$$

$$L_s = L \left( \frac{Q^2}{1+Q^2} \right)$$

$$Q_L = \frac{R_L}{\omega L_1} = \frac{\omega L_s}{R_{des}} = \frac{1}{\omega C_1 R_{des}}$$

$$C_1 = \frac{1}{\omega R_{des} Q_L} = \frac{1}{2\pi \times 10^9 \times 3.125 \times 4.45142}$$

$$C_1 = 1.14412 \times 10^{-11} \text{ F} = 11.4412 \text{ pF}$$

$$L_s = \frac{1}{\omega^2 C_1} = \frac{10^{12}}{4\pi^2 \times 10^{18} \times 11.4412} \text{ H} = 2.21395 \text{ nH}$$

$$L = L_s \left( \frac{1+Q_L^2}{Q_L^2} \right) = \cancel{2.23} 2.32568 \text{ nH}$$

$$L = L_1 || L_2 = \cancel{1.99887 \times 10^{-9} \text{ H}}^{2.07 \text{ nH}}$$

$$L = \cancel{1.9989 \text{ nH}} 2.07 \text{ nH}$$

Simulation Results:


$$BW = \frac{204.125}{209.563} \text{ MHz}$$

$$Q = \frac{1 \text{ GHz}}{BW} = \cancel{4.772} 4.899$$


$$S_{dB} @ 1 \text{ GHz} = \cancel{-20.25} -60 \text{ dB}$$

T-match parameters:
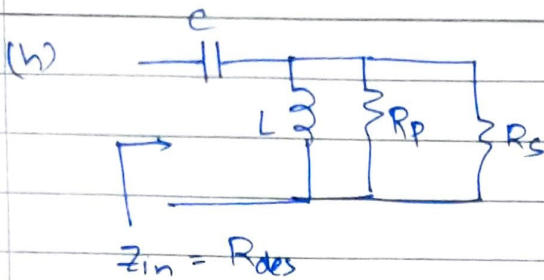
$$L = 1.999 \text{ nH}, C_1 = 11.4412 \text{ pF}, C_2 = 5.8023 \text{ pF}$$



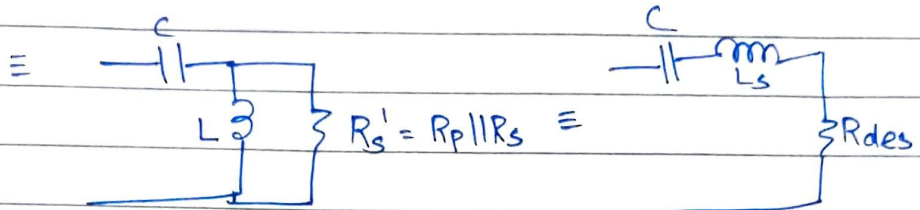$Q = \frac{R_p}{\omega L}$   
 $R_p = 15\omega L$



$R_p || R_s = R_s'$   
 $R_{des} = \frac{R_s'}{1 + Q^2}$

For  $L = 2.0547 \text{ nH}$ ,  
 $R_p = 193.651 \Omega$

$Q = \frac{R_s'}{\omega L} = \frac{\omega L_s}{R_{des}} = \frac{1}{\omega C R_{des}}$

$R_s' = \frac{50 \times 15\omega L}{50 + 15\omega L} = \frac{4.71239 \times 10^{12} L}{50 + 9.4248 \times 10^{10} L}$

$Q = \frac{\sqrt{R_s' - 1}}{\sqrt{R_{des}}} = \frac{\sqrt{1.50796 \times 10^{12} L - 50 - 9.4248 \times 10^{10} L}}{\sqrt{50 + 9.4248 \times 10^{10} L}}$

$Q = \frac{\sqrt{1.4137 \times 10^{12} L - 50}}{\sqrt{9.4248 \times 10^{10} L + 50}} = \frac{\sqrt{2.8274 \times 10^{10} L - 1}}{\sqrt{1.88496 \times 10^9 L + 1}}$

$C = \frac{1}{\omega R_{des} Q} = \frac{1}{2\pi \times 10^9 \times 3.125 Q}$

$C = \frac{1}{\sqrt{\frac{1.885 \times 10^9 L + 1}{2.827 \times 10^{10} L - 1}}} \times \frac{1}{1.964 \times 10^{10}}$

$L_s = \frac{1}{\omega^2 C} = \frac{\sqrt{2.827 \times 10^{10} L - 1}}{1.885 \times 10^9 L + 1} \times \frac{1.964 \times 10^{10}}{4\pi^2 \times 10^{18}}$

$L_s = \frac{\sqrt{2.827 \times 10^{10} L - 1}}{1.885 \times 10^9 L + 1} \times 4.975 \times 10^{10} \text{ H}$

$L = \frac{R_s' R_{des}}{\omega^2 L_s} = L_s \left( \frac{1 + Q^2}{Q^2} \right)$

$L = 4.975 \times 10^{10} \left( \frac{3.0155 \times 10^{10} L}{\sqrt{1.885 \times 10^9 L + 1}} \times \frac{1}{\sqrt{2.827 \times 10^{10} L - 1}} \right)$

$\Rightarrow (1.885 \times 10^9 L + 1)(2.827 \times 10^{10} L - 1) = 2.47506 \times 10^{19} \times 225.063$



$$5.3289 \times 10^9 L^2 + 2.6385 \times 10^0 L - 226.063 = 0$$

$$L = 1.8269 \text{ nH} \text{ or } L = -2.322 \text{ nH (x Capacitive)}$$

$$L = 1.8269 \text{ nH}$$

$$R_p = 15 \times 2\pi \times 10^9 \times L = 172.181 \, \Omega$$


$$Q = 3.3763$$

$$C = 15.0844 \text{ pF}$$

Simulation Results:

$$BW = 274.632 \text{ MHz}$$

$$Q = 3.64$$

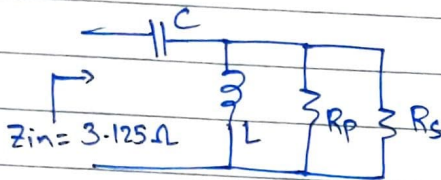

(g) With noise:

$$R_p = 193.651 \, \Omega$$

$$L = 2.0547 \text{ nH}$$

$$C = 13.15 \text{ pF}$$

$$BW = 307.6932 \text{ MHz}$$

$$Q = 3.249$$

## Result Waveforms

### L-Match Network

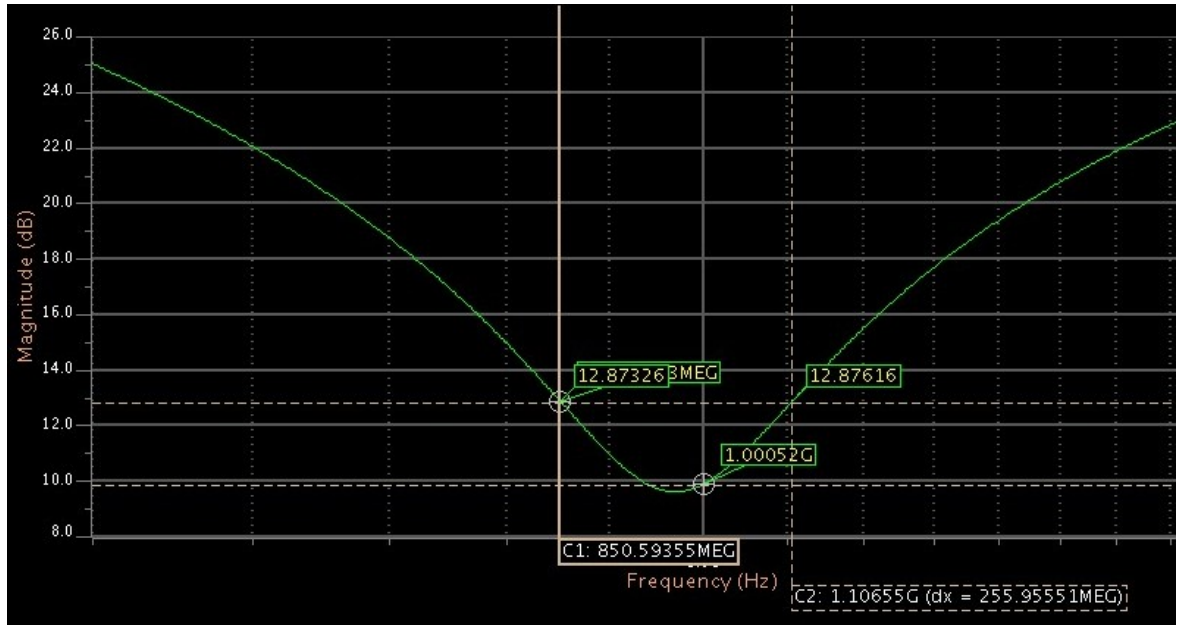


Figure 1:  $Z_{dB}$  of L-match network.  $BW = 255.956$  MHz,  $Q = 3.9069$ .  
 $Q_{theoretical} = 3.873$


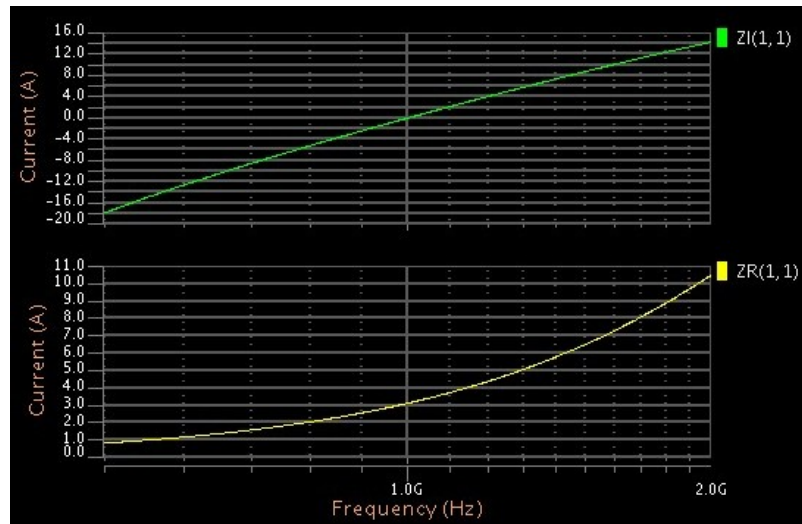


Figure 2:  $Z_{in}$  of L-match network.  $Z_r \approx 3.125\Omega$ ,  $Z_i = 0\Omega$  at 1GHz

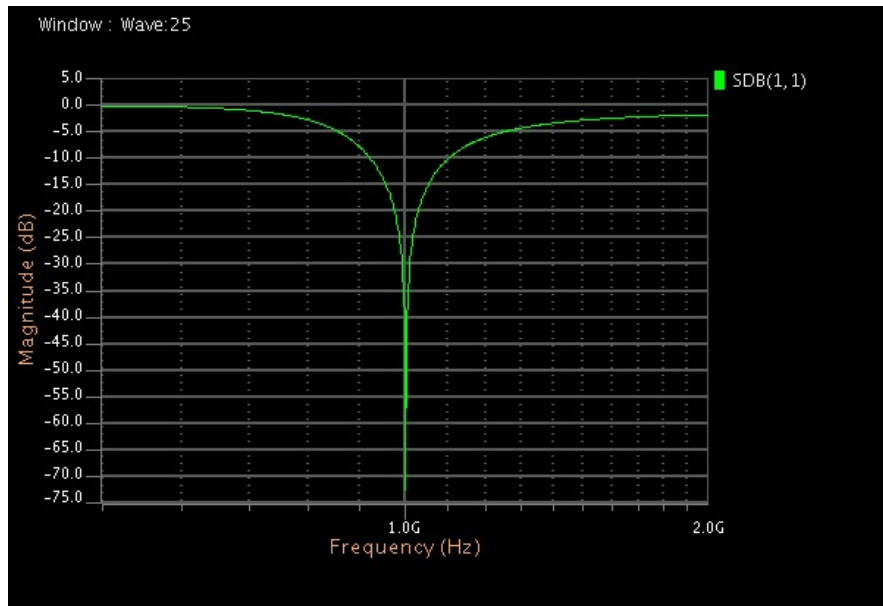

Figure 3:  $S_{dB}$  of L-match network.

## T-Match Network

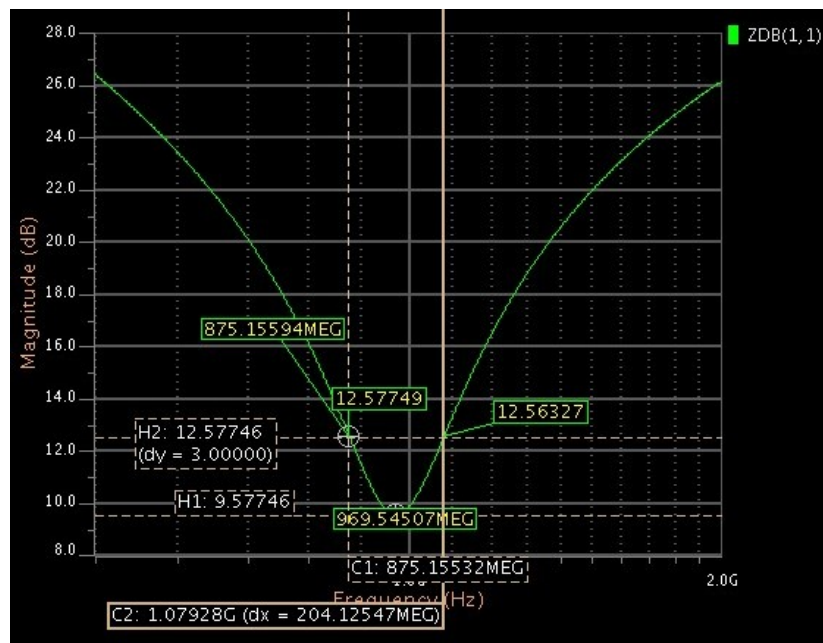


Figure 4:  $Z_{dB}$  of L-match network.  $BW = 204.125$  MHz,  $Q = 4.899$ .  
 $Q_{theoretical} = 5$

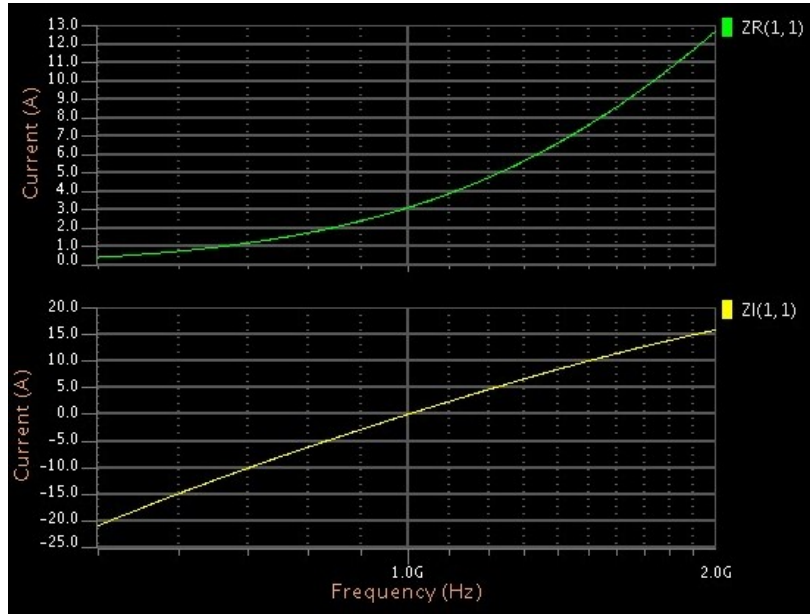


Figure 5:  $Z_{in}$  of T-match network.  $Z_r \approx 3.125\Omega$ ,  $Z_i = 0\Omega$  at 1GHz

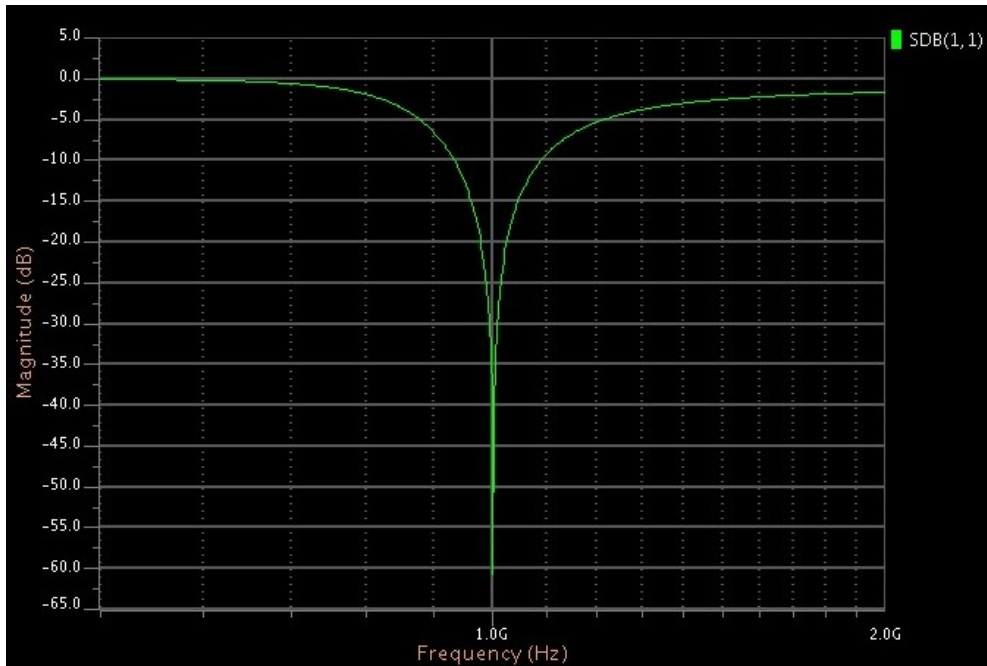


Figure 6:  $S_{dB}$  of T-match network.

## L-Match with Noisy Inductors

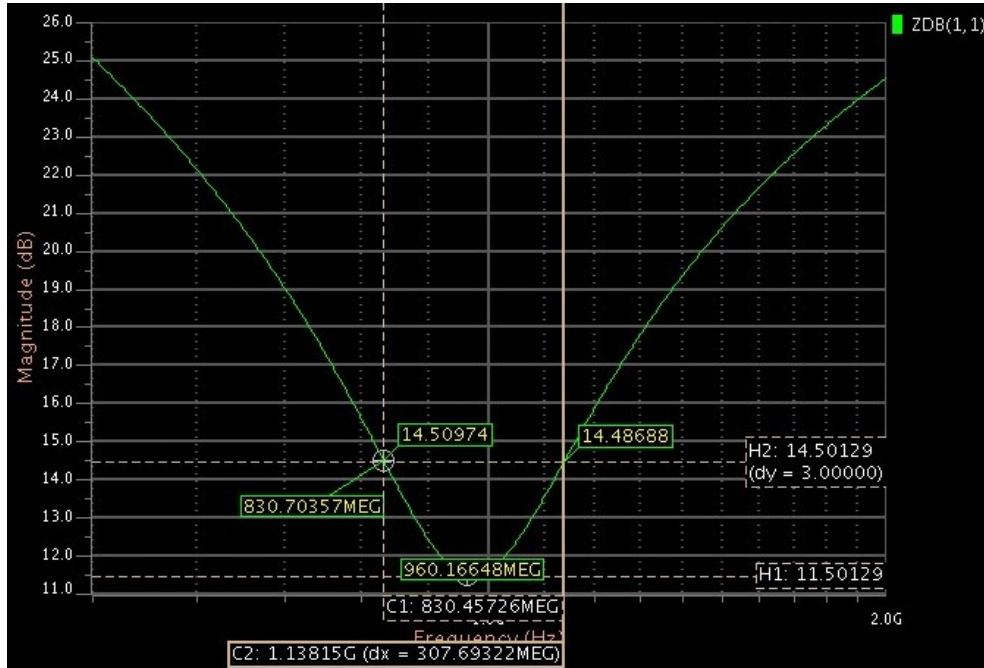


Figure 7:  $Z_{dB}$  of L-match network.  $R_p = 193.651\Omega$ ,  $BW = 307.693$  MHz,  $Q = 3.249$ .  $Q_{theoretical} = 3.873$



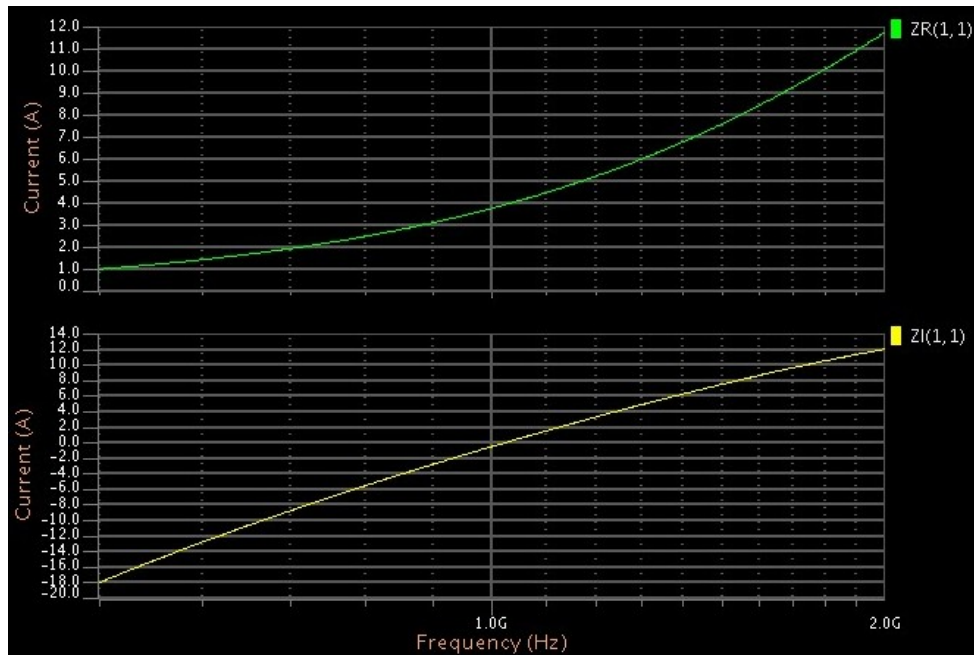


Figure 8:  $Z_{in}$  of L-match network. Notice deviation from desired values

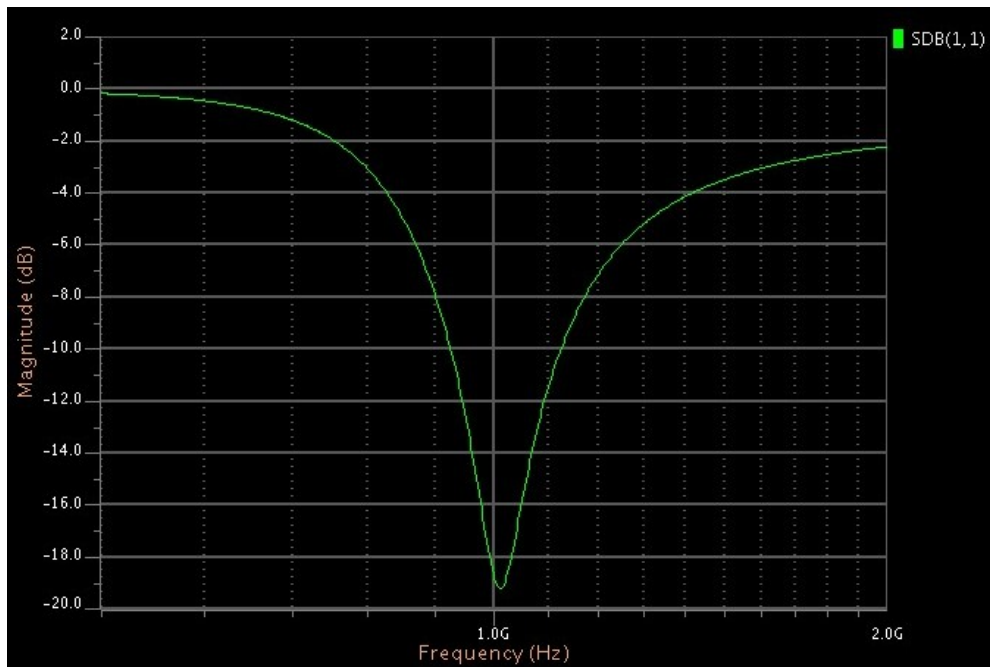


Figure 9:  $S_{dB}$  of L-match network. The minima in  $S_{dB}$  is now shifted away from the operating frequency, and is only  $\approx -19dB$

## Optimised L-Match Network accounting for Noisy Inductors

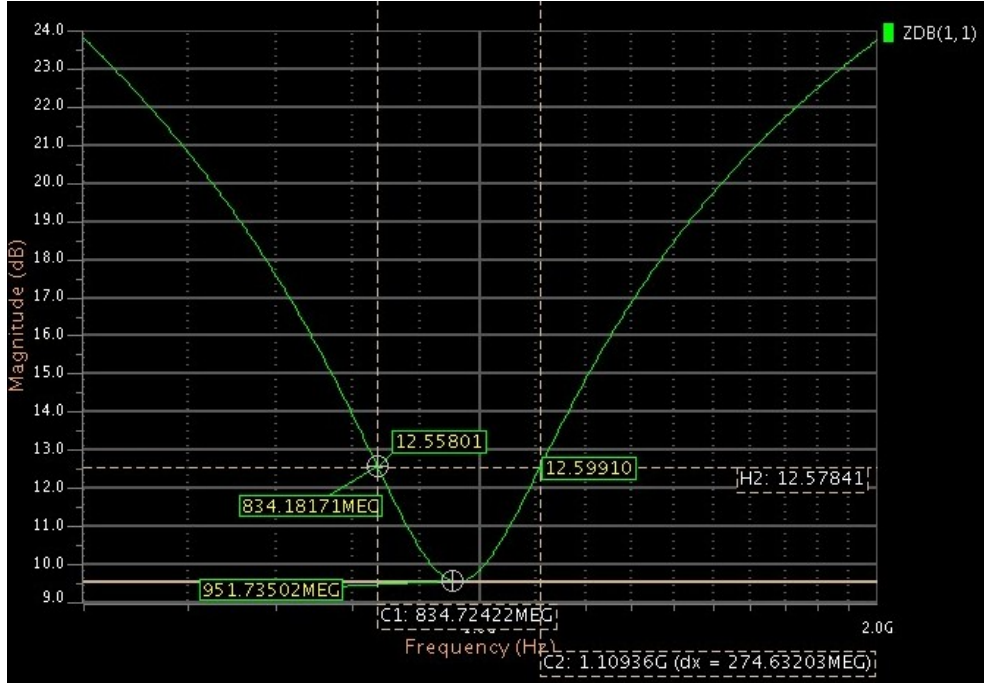
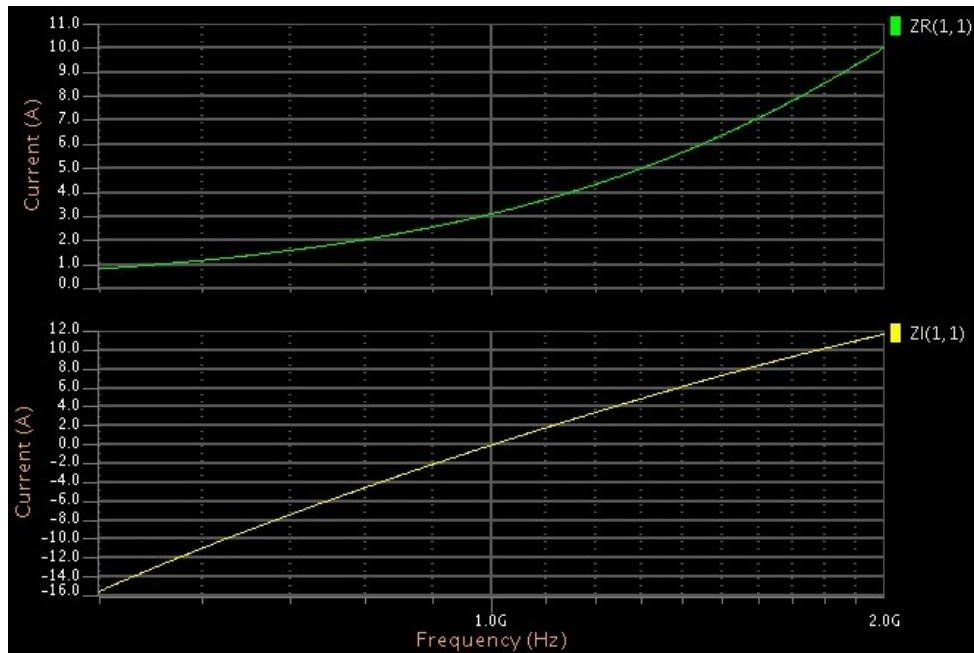
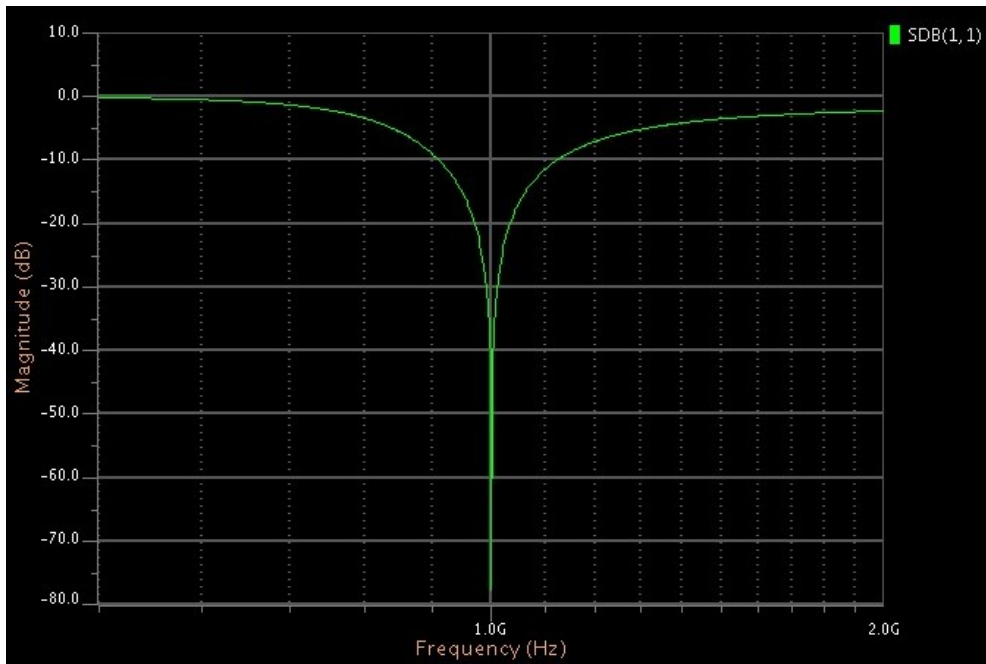


Figure 10:  $Z_{dB}$  of L-match network.  $R_p = 172.181\Omega$ , BW = 274.632 MHz, Q = 3.64

Figure 11:  $Z_{in}$  of L-match network.Figure 12:  $S_{dB}$  of L-match network.

\*\*\*